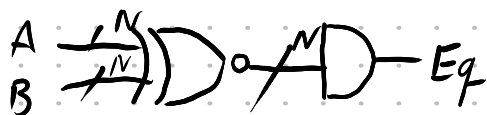


Compare Eq:



$$Eq = \&(\sim(A \wedge B))$$

Compare Lt:


overflow detection for subtraction

- $\&$  - opposite signs for A and B  $(A[N-1] \wedge B[N-1])$
- $\&$  - opposite signs for sum and A  $(A[N-1] \wedge Sum[N-1])$

$$V = (A[N-1] \wedge B[N-1]) \& (A[N-1] \wedge Sum[N-1])$$


According to HLT, for 2 signed numbers
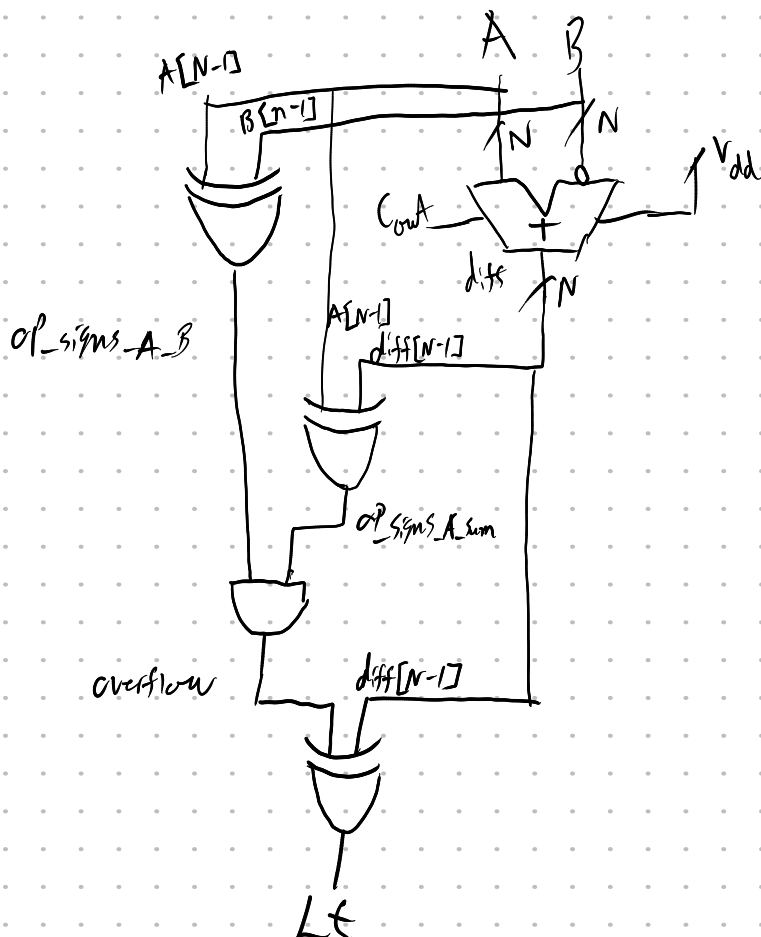
$$L = V \wedge N \quad N = Sum[N-1], \text{ negative output}$$



# Pulse Generator

ticks = 4

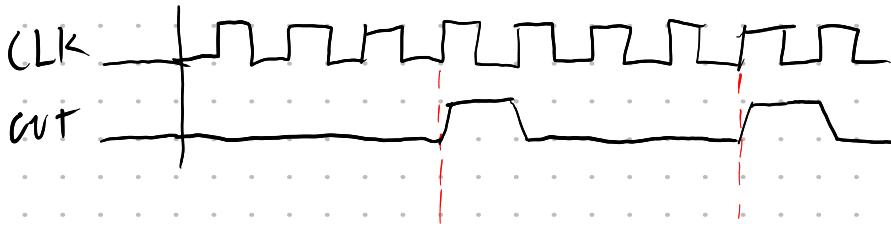


Counter:

output: if count == ticks 1  
else 0

Use >= increase ticks is changed

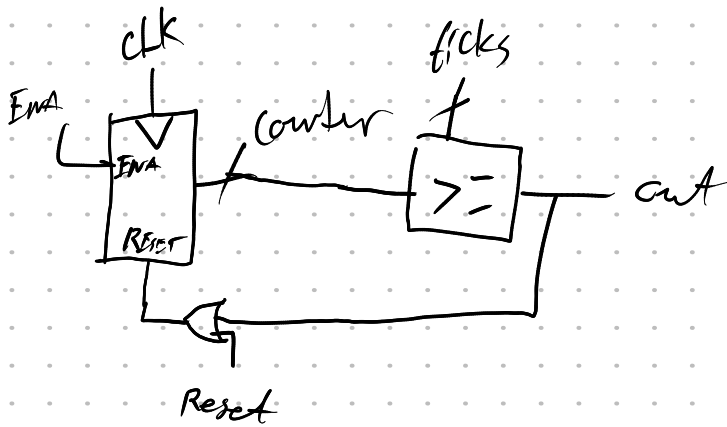Next state if count >= ticks 0  
else counter++



Reset

using counter module

